

# Introductory Experiments and Linear Circuits I

Jung Lin (Doris) Lee [Lab Partner: Leah Tom]  
Prof. William Holzapfel, GSI Thomas Darlington, Thomas Mittiga, John Groh,  
Victoria Xu, Jonathan Ma, Francisco Monsalve, Xiaofei Zhou

January 30, 2015

## Abstract

In this lab, we explore — BSC

## 1 Introduction

1.2

1.4

## 2 Keithley 2110 Digital Multimeter<sup>3</sup> (DMM)

- uncertainty The range should be adjusted suitable range within — for each measurement , within order of magnitude. <sup>1</sup>

## 3 BSC Laboratory Breadboard Box

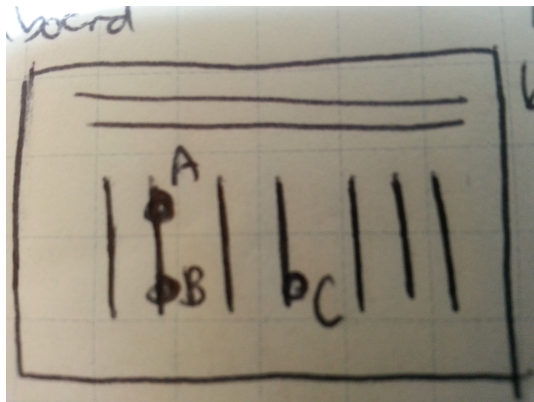


Figure 1: We put jumper wires connecting the A and B, B and C separately and measure the resistance across them.

---

<sup>1</sup>Too large a range will result in the error “OVLRD” (overload) and too low will cause —

**1.1** The breadboard is a device suitable for rapid-prototyping circuits, without long chemical etching process of the PCB. As shown in Fig.1 , it is horizontally connected along the longer edge for the two top and bottom buses, which often serves as to input voltage and grounding -. We measured the resistance across A and B as  $0.16\ \Omega$  and across B and C as “overload”. These result make sense because since B and C is not connected, the resistance is almost infinite, and is therefore not registered on the DMM. Likewise, since A and B are connected, there is minimal resistance between them.

**1.3** The reading between the 12 output and the 5V supply ground fluctuates around 0V. The reason why —.

**1.5** Since the resistors are arranged in series as shown in Fig.2, the current through each resistor should be the same.

$$I = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2} = \frac{24V}{480 \times 10^3 \Omega} = 5/0 \times 10^{-5} A \quad (1)$$

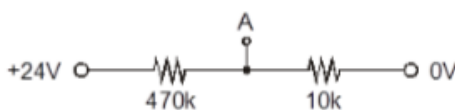


Figure 2: Voltage divider setup

**1.7** a) Depending on the DMM setup, it can act as a voltmeter or ammeter. To meaasure the current through a  $10k\Omega$  resistor, we need to connect the DMM in parlalle with the  $10k\Omega$  resistor as shown in Fig. — Then, using Ohm’s law we can compute the current flowing through the  $10k\Omega$  resistor:

$$I = \frac{V}{R} = \frac{0.510V}{10k\Omega} = 5.1 \times 10^{-5} A \quad (2)$$

which is approximately the same as predicted in 3. Alternatively, we can also connect the multimeter in series with the resistor as shown in Fig. 3 <sup>2</sup> to measure the current directly, and this yields the same current value as computed in Eq.2. b)



## 4 Digital Oscilloscope

voltage on the vertical axes and time on the horizontal axes

### 4.1 Tune-able Parameters and useful functions

- AC/DC Setting : (See Sec.6.1)
- Scale: Vertical and horizontal zoom in ; adjust accordingly to — window that best captures
- Measurement: useful quantities

---

<sup>2</sup>Note that the — terminate need to be plugged into the hole that — and — instead of the — and — as when we do the voltage measurement. The left 2 — gives a better accuracy

## 5 Arbitrary Waveform Function Generator

## 6 Frequency and time measurements

### 6.1 AC measurement

## 7 Thevinin Equivalence

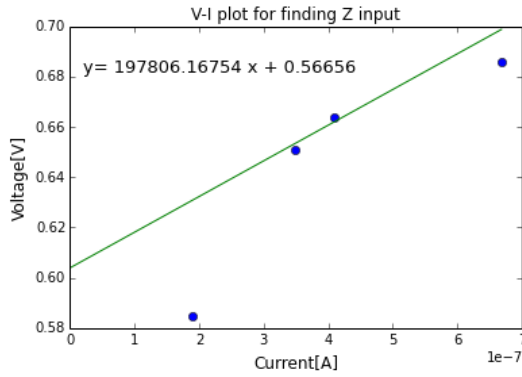
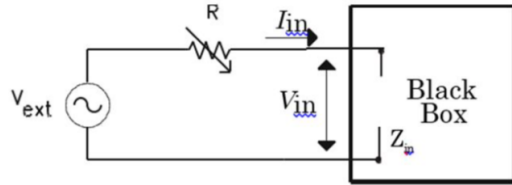


Figure 3: Voltage measurement has uncertainty of 0.001V .

**2.3** We treat the oscilloscope as a black box of unknown impedance. We substituted different resistors in the circuit shown in Fig.7, and measured the input voltage. Using Eq.3 , we can compute the input current as plotted in Fig. 3

$$I_{in} = \frac{V_{ext} - V_{in}}{R} \quad (3)$$

A linear regression on the data results in a slope of 0.197806 M $\Omega$ . Since  $Z_{in} = \frac{V_{in}}{I_{in}} R = \frac{V_{in}}{V_{ext} - V_{in}}$ , the value of the slope is equivalent to the input impedance, which is the same order of magnitude as the input impedance of typical oscilloscope (  $\approx 1$  M $\Omega$ ). [? ]

## 8 Conclusion

## 9 Acknowledgments

The author would like to acknowledge support from the GSI in — this lab —. I thank my partner, Leah Tom, for helpful discussion and — collaboration that helped this work.