

Lab 8 : Op Amps III

April 6, 2015

Jung Lin (Doris) Lee [Lab Partner: Leah Tom]

Prof. William Holzapfel, GSI Thomas Darlington, Thomas Mittiga, John Groh,
Victoria Xu, Jonathan Ma, Francisco Monsalve, Xiaofei Zhou

Introduction

In our final lab on op amps, we investigate how op amps can deviate from its expected behavior to the golden rules. We investigate common imperfections in op amp circuits such as distortions and noises. In addition, we learn how a bipolar junction transistor (BJT) works and how they can be used in circuits. We use circuit simulation programs to learn about how noise is generated and analyze the AC behavior of the components. Most importantly, we learn how these imperfections can be eliminated or alleviated in order to attain a T_2 audio signal with good sound quality.

8.1

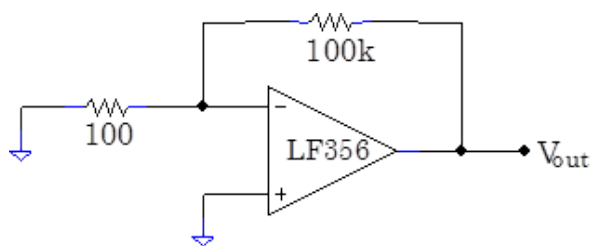


Figure 1: Circuit Schematic for the inverting amplifier

We built the inverting amplifier as shown in Fig.1 and measured the output voltage. We computed the input offset voltage by:

$$V_{os} = \frac{-10.8}{1000} = 0.0108V \quad (1)$$

To see whether this varies greatly for different op-amps, we conducted the same measurements for four other op amps, and obtained a V_{out} of 452 ± 0.074 mV, 1.28 ± 0.0081536 mV, -1.03 ± 0.0081236 mV, and 1.08 V ± 0.3296 mV. There is order-of-magnitude variations in the offset voltage of different op amps.

8.2

We built the Fig.2 circuit for removing the input offset. Using the op-amp from question 1 which had an input offset voltage of 1.08m, we know that it has a corresponding V_{out} of 1.08V. We adjusted the potentiometer until the scope reads a V_{out} value of 2.24 mV ± 0.04 mV. After adjusting, the output was observed to drift between 1.88mV and 6.74mV. A possible reason for the drift could be due to an unsteady power supply or noise from the environment.

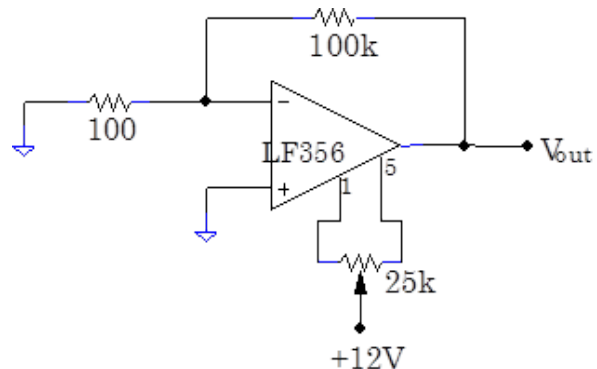


Figure 2: Circuit Schematic for removing input offset.

8.3

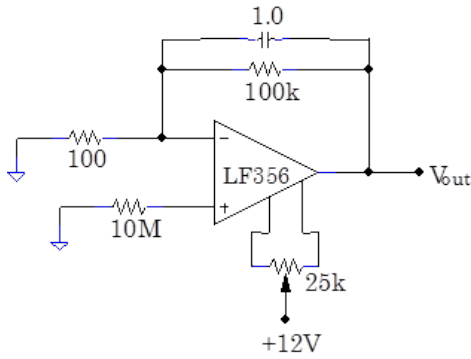


Figure 3: Circuit Schematic for measuring the input current bias.

We construct the circuit as shown in Fig.3. When we short the 10M Ω resistor, the minimum V_{out} measured is 1.88mV \pm 0.04mV. When we removed the shorting wire, we measured a mean voltage of -120mV \pm 0.05mV. The output voltage is a periodic wave with V_{pp} = 320mV. The input bias current (I_B) is computed as:

$$I_B = \frac{\Delta V}{10M\Omega} = -1.22 \times 10^{-8} A (3s.f.) \quad (2)$$

8.4

We drove the follower shown in Fig.4 with a 10 V $_{pp}$, 1kHz triangular wave. We tried using different values of R_L and found that as we increase the resistance the output current increases, so the output current does depend on the load resistance. The output current reaches a maximum when the resistance is around 5k Ω . In looking at the scope traces, we found that at low resistance, the wave is more distorted than at high resistance.

8.5

We built the amplifier as shown in Fig.5. Feeding in different functional waveforms

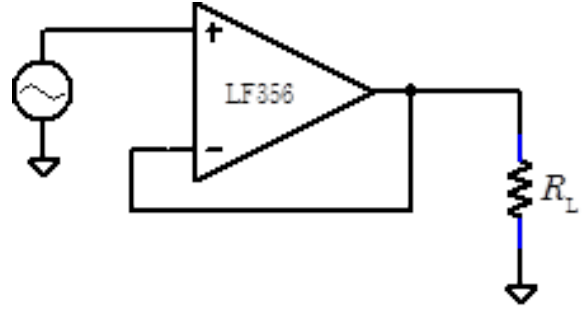


Figure 4: Circuit Schematic for the inverting amplifier

as V_{in} with V_{pp} as 1.00 V and a frequency of 1Hz, we find that the sine wave has the lowest pitch, and the square wave sounds slightly higher. The triangular wave has a distinguishably much higher pitch and sounds sharp to the ear.

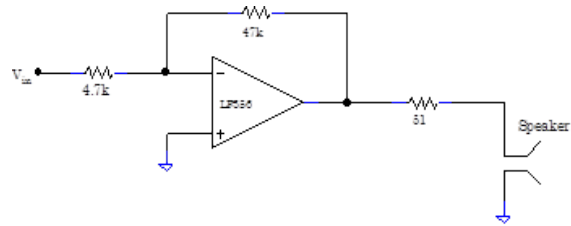


Figure 5: Circuit Schematic for the audio amplifier.

The maximum amplitude that we can drive the speaker without distortion is 320.0 mV $_{pp}$. The volume lowers when we decrease the amplitude. Using the T_2 audio output, we obtained a sound of acceptable quality but not of the clearest sound quality.

8.6

Using a sine wave input, we find that the volume increased as we increased the input amplitude from 0.01 to 1V. When the amplifier is driven by T2, the sound quality is poor. The speaker only emits a pure sine note at 20mV $_{pp}$ as observed from the scope traces. Sketches of the output waveforms

as shown in Fig.6. As the amplitude is increases, the output waveform becomes more distorted and the lower part of the sine wave gets more rectified.

8.7

We try to improve the follower's performance by including a feedback loop in the circuit, so that it takes a larger input amplitude to distort the waveform. In this circuit, sine wave gets distorted beyond input amplitude of 270mV_{pp} . The circuit can amplifying triangular waves without distortion as shown in Fig.7 with a tolerance of a higher amplitude. On the other hand, we find that the square wave gets distorted and exhibits sharp peaks when the signal's sign changes, while retaining the general waveform of a square wave.

8.8

We used the FollAmp Multisim program to compare the follower circuits in 8.6 and 8.7.

There is an offset for circuit in 8.6 because the feedback loop is connected directly to the output and so the output at the speaker has a DC offset because of the $+12\text{V}$ and -12V supply the op-amp connects to, which isn't accounted for by the feedback loop. The offset is smaller but not completely gone for the circuit in 8.7 because the feedback loop doesn't work perfectly because there are limitations to the op-amp.

The half wave distortion for both circuits happens at 0.25V because the circuit cannot accommodate very negative signals because the BJT is only forward conducting. The gain of 8.7 is better than that of 8.6 because the feedback loop in 8.7 accounts includes

the 100Ω resistor and since there is no voltage drop across that to account for, the output voltage measured is greater in 8.7.

8.9

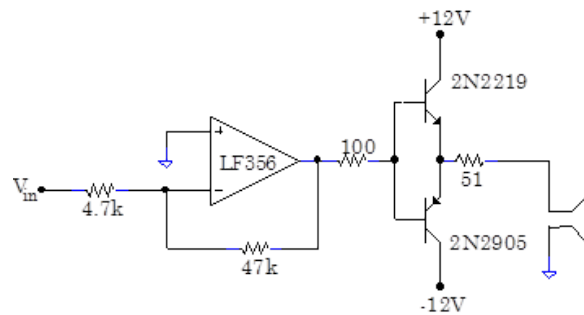


Figure 9: Circuit Schematic of the follower circuit.

We built the circuit shown in Fig. 9 and fed in a 500Hz sine wave of different amplitudes. As shown in the scope traces in Fig.10, we find that the crossover distortion near the x axis is most evident in the 0.15 and 1.5V_{pp} cases. We also find that the crossover distortion is more evident at very high frequencies, since the transistor is out of its operating range.

Crossover distortion happens when the signal goes from one device to another. In Fig.1, the signal crosses over from the upper BJT to the lower BJT. For the top BJT the voltage across the base and emitter (V_{BE}) is a nonzero value, so the signal will not go through unless the input signal is smaller than V_{BE} . Likewise, this also happens when the upper transistor stops passing through current and the current goes through the lower portion and also feeds to the load (50Ω resistor and speaker). Therefore, in the $V=0$ region the transition stops at a value to the right and left of the original zero point, resulting in the "kink" in the crossover region.

Then, we change the connection of the $47\text{k}\Omega$ to be on the node leading the 51Ω re-

sistor that protects the speaker, as illustrated in Fig. 11.

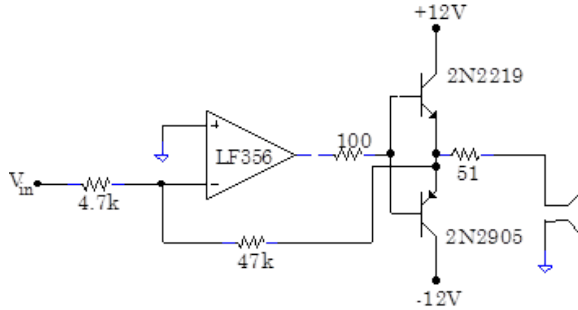


Figure 11: Circuit Schematic of push-pull feedback circuit.

As evident from the scope traces in Fig. 10, we find that the crossover distortion is diminished when compared with the scope trace of the same amplitude settings. Using the T_2 audio signal, we find that the sound quality is slightly better in the circuit in Fig.11.

8.10

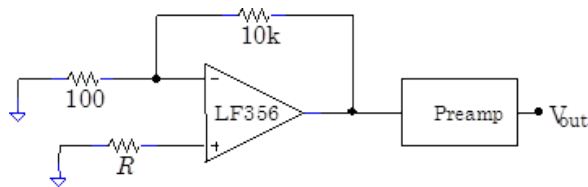


Figure 12: Circuit Schematic for measuring RMS noise.

We setup the circuit as shown in Fig.12, with the preamp gain set to 100, low pass and high pass filter set to 100kHz and 1kHz respectively. With $R=0$, we used the DMM and measured $16.024 \pm 0.0059 \text{ mV}$. Using the scope measured a V_{pp} of 124mV, so the noise is computed as $124 \text{ mV} / 6 = 20.7 \pm 0.0065 \text{ mV}$.

To measure the Johnson noise generated by the resistor, we attached the $1 \text{ M}\Omega$ resistor and again measure using both the oscilloscope and DMM method. Using the DMM,

we measure $0.6698 \text{ V} \pm 0.4804 \text{ mV}$ and using the oscilloscope we measured $4.40 \text{ V} / 6 = 0.733 \text{ V} \pm 0.4879 \text{ mV}$. We eliminated the possibility that this is due to the line (60Hz) noise in the environment because we don't see a distinguishable sine wave on the scope traces.

8.11

The generator still generates a Gaussian distribution everytime we do a generate spectrum because a inverse Fourier transform of a Gaussian function is still a Gaussian function, as shown in Fig.13 . Uniform white noise sounds like the Gaussian noise, but the volume is slightly louder. The $1/f$ noise does sound like a distant ocean wave, with a lower sound volume.

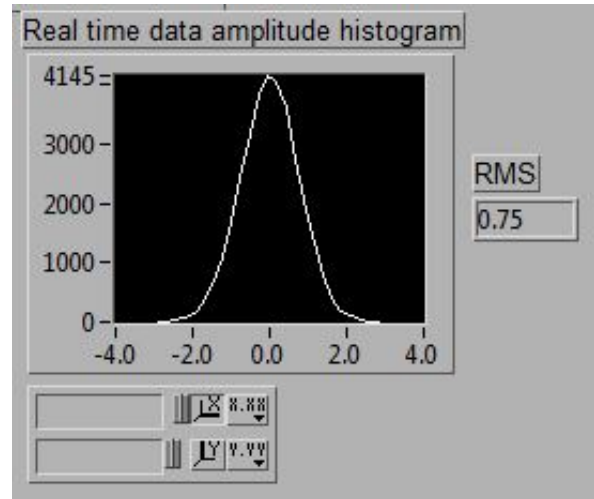


Figure 13: Amplitude histogram of Gaussian noise.

We find that if we alter the low-pass frequency, it cuts away the high frequency noises. When we generate a spectrum as a superposition of many low frequency waves, then the audio rfrequency sounds lower (like a furnace) since only the low frequencies below 500 Hz can pass through the filter as shown in the Fig. 14.

When the average number of shots per sample is set as 0.0010, the arrival time of

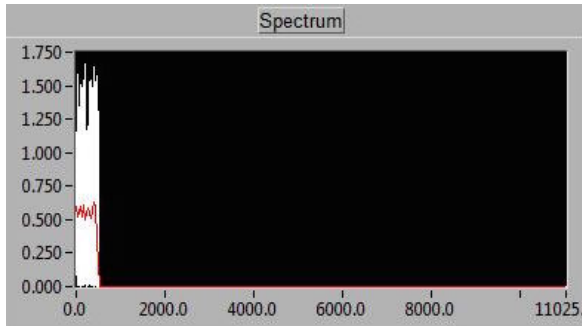


Figure 14: Low pass frequency set as 500 Hz.

the particle on the detector sounds discrete, like a popping sound of the radio when it is not tuned at a channel. We tried setting the average number to larger numbers and the sound became more continuous and sounding like Gaussian noise. This corresponds to the histogram shown in Fig.16

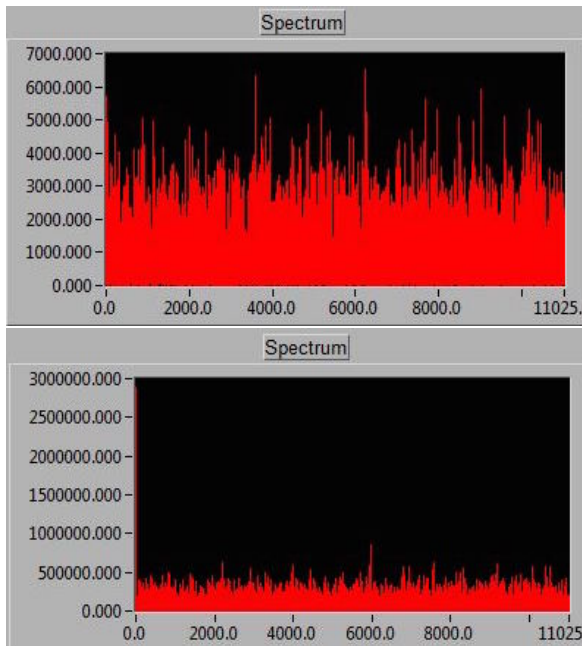


Figure 15: The average number of shots per sample can be estimated from the y-axis as the mean of the spectrum. [x: frequency ; y: number of shots]

In addition, as we increase the average number of shots, the volume also decreases because when there is greater number of peaks

added up together. The superposition of the wave diminishes the variation of the waves (even though it provided a larger offset). Since amplitude measures the difference between the peak and trough of the wave, the volume decreases as we increase the average number of shots.

For the line noise, at low harmonic content, the sound is smooth, but begins to get noisy as harmonic content exceeds 0.8. This is because it is now composed of more frequency components, as shown in Fig.17. The sound of the line noise sounds like the buzzing 60 Hz noise of common electronic appliances such as an old CRT TV monitor.

8.12

Using Multisim, we simulate the circuit shown in Fig. 18: We conduct a AC analysis

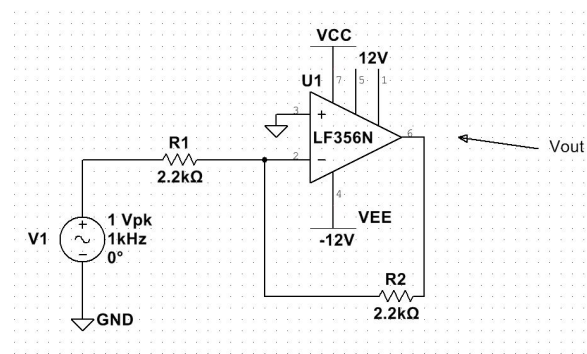


Figure 18: Circuit schematic

by examining how the LF356 responds to different frequencies. We consider only the behavior in the frequency range of 0 to 100 kHz, (operating range of the op amp). From Fig.19, we subtract the difference between the V_{out} and V_{in} and obtained a phase shift of about 180 degrees. In the operating range, V_{out} and V_{in} are approximately equal so the gain is about one.

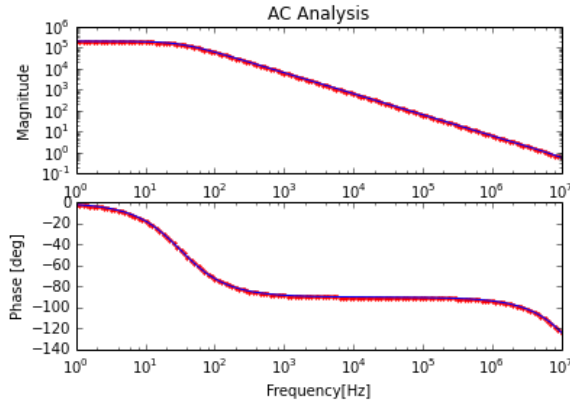


Figure 19: Frequency response of circuit based on V_{out}/V_2 . Above: Magnitude plot. Below: Phase shift plot

8.13

We constructed the differentiator as shown in Fig.20. By measuring the output signal on the oscilloscope, we find that the output waveform is sinusoidal with a frequency of 2.23kHz. The sine wave is modulated by another wave with a lower frequency. Despite the grounded input and decoupled capacitors to prevent parasitic oscillation, the output signal still fluctuates greatly.

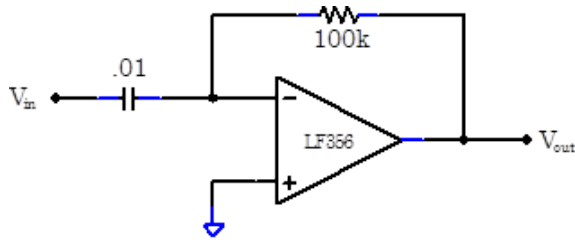


Figure 20: Circuit Schematic for the differentiator.

This behaviour is explained by the fact that there is a phase shift between the signal from ground to the input after passing through capacitor and the ground. To compensate this effect, V_{out} has a phase shift from the input which creates potential difference, causing the oscillations we see in Fig.21. Because the capacitor introduces a

$\pi/2$ phase shift between the input and output signal, the circuit is able to differentiate its input. Mathematically, the phase difference between a cosine and sine is $\pi/2$, so if we were to model the input wave as sine wave, then the output wave would be a cosine wave and vice versa. This yields a differentiated output signal.

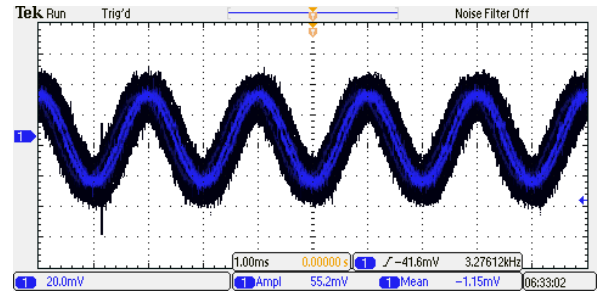


Figure 21: Scope traces showing signal from a differentiator.

8.14

Compared to the differentiator in 8.13, this circuit is more stable and fluctuates to a lesser extent. This improvement is due to the addition of a capacitor between the input and output, which acts as a bypass filter for any oscillating signals in the background. When varying the frequencies and taking measurement on the oscilloscope, we obtained the transfer function and the phase difference as plotted in Fig.22.

8.15

We drove an op amp follower as shown in Fig. 4. As shown in the scope trace in Fig.23, the slew rate is the maximum rate of change of output voltage per unit of time. We compute the slew rate as:

$$\frac{20.6V}{0.6div \times 2.00\mu s/div} = 17.1V/\mu s \quad (3)$$

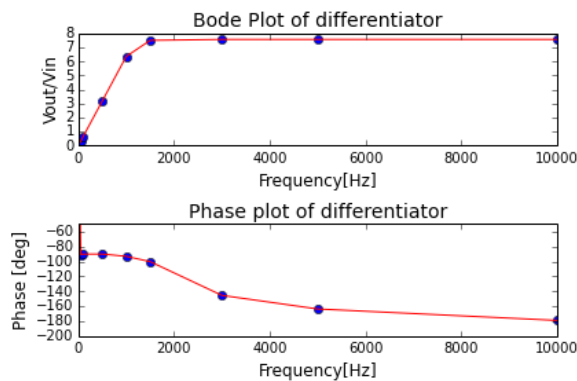


Figure 22: Above: Bode plot of differentiator; Below: Phase difference plot. We find that the gain increases linearly between the range of 0 and 2kHz and then flattens out at around 5kHz. The circuit differentiates signals with frequencies between 0Hz and around 1400Hz.

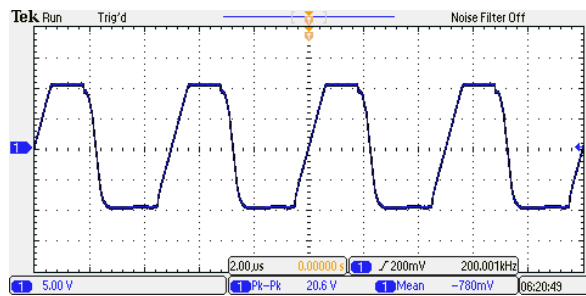


Figure 23: Scope trace for measuring slew rate of op amp follower.

8.16

If we change the follower's emitter resistor to 51Ω , then we can draw a large amount of current to the input, since this resistor is now comparable to the resistor in series with the speaker. Using Joules' heating law, ($P = I^2R$) the decrease in current results in a decrease in power through the speaker. Thus, the speaker does not have enough power to make a sound. This will not work in the real world because the circuits in question 8.6 and 8.7 cannot accommodate very negative signals.

The push-pull circuit in question 8.9 averts this issue by using two BJT in series rather

than a single BJT in the 8.6 and 8.7 circuits. This configuration works even when there is a negative signal, since the bottom BJT becomes conducting for a negative input. Likewise, when there is a positive signal, the top BJT becomes conducting. Treating our resistor and speaker as the load, we find that the top and bottom BJTs act alternately as a sinking and sourcing current. One "pushes" the current towards the load and another "pulls" it back. As a result, an alternating signal can be used to power the speaker, for both a negative and positive input. Since audio signals consist of both positive and negative wave signals, this proves to be a better circuit for playing audio, rather than cutting away the negative component of the wave signal as did the other circuits.

8.17

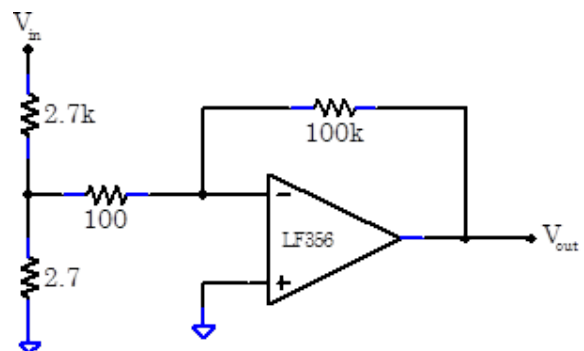


Figure 24: Circuit schematic for the inverting amplifier.

We constructed the circuit as shown in Fig.24. We drove the circuit with a variety of frequencies in the range of 100 Hz to 10 MHz. We measured V_{out} and V_{in} to compute the gain and the phase difference on the oscilloscope. We find that the phase decreases from -180 deg to about -90 degrees before increasing again.¹ For the gain

¹Note that in the last two measurement

measurements, the values increases initially but beyond 1kHz the gain decreases as frequency increases.

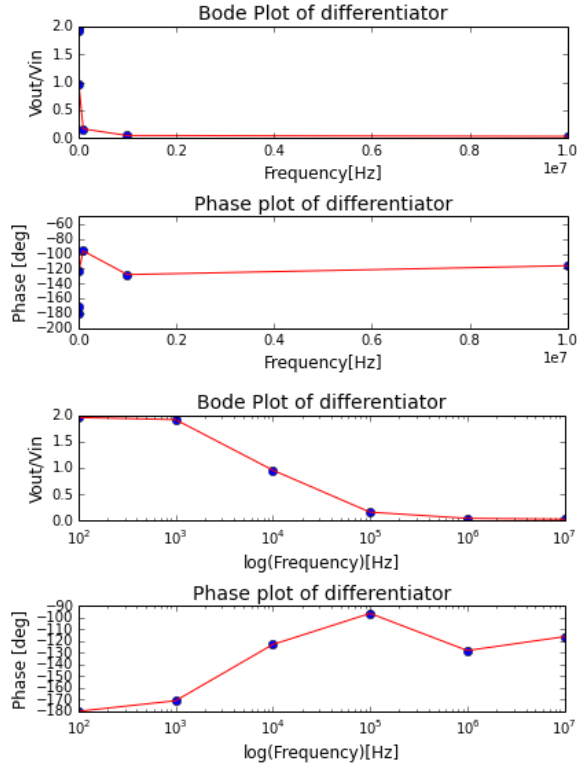


Figure 25: Bode and phase plots for the differentiator. Top 2: Linear scale. Bottom 2: Log of frequency in the x axis (since the data was taken geometrically).

8.18

We construct the Fig.27 circuit and drove a $0.5V_{pp}$ sine wave. We measure the gain and the phase difference between the input and output as plotted in Fig.??.

The gain initially decreases with frequency. After the kink around 10^5 Hz, the frequency increase again. There is a constant $\pi/2$ phase difference between the input and the output

(1MHz,10MHz), the phase measurement fluctuated greatly. So the value that we recorded is not very reliable.

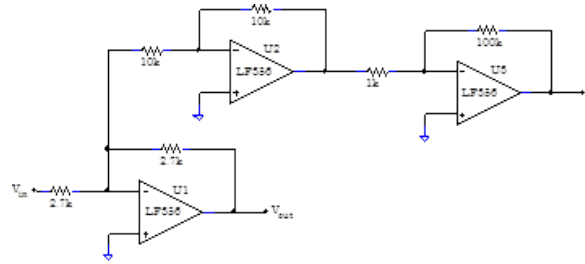


Figure 26: Circuit schematic for the 8.18 module.

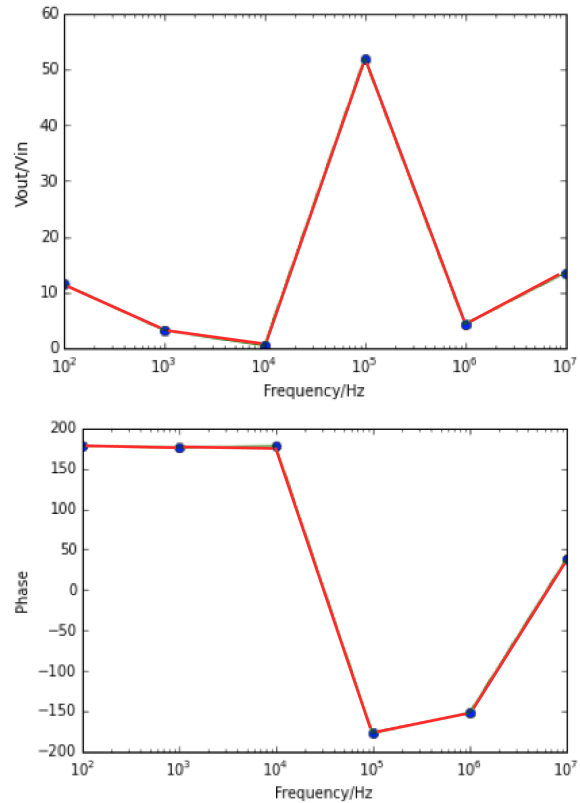


Figure 27: Top: Bode plot. Bottom: Phase plot.

initially, which drops and reverses to $-\pi/2$ as frequency increases. Then, the magnitude of the phase drops to 0 with further increases in frequency.

Because of the constant sign-switching at the U1 input at high frequencies, it is hard to detect the phase shift even though there is supposed to be a phase difference between the input and the output. So when we connect the input into a unity gain op-amp, and

measure the V_- at the output of that op-amp, we are able to measure a steady output, with a reliable phase shift measurement.

At low frequencies, it is hard to accurately measure the input voltage, as the gain is very large. Therefore, we use U3 to amplify the input signal so that we can measure V_- more accurately at low frequencies.

U2 acts as a unity gain op-amp that is present so we can measure phase of the input signal more accurately. Due to the feedback loop in U1, there can be interference from the output interfering with the input measurement. We have to add another op-amp to compensate for this effect.

We cant use U3 at high frequencies because the phase shift falls to -90 deg across one op-amp for higher frequencies as seen in 8.17. Hence, since the input signal is going through 2 different op-amps before being measured, the phase shift measured will be inaccurate. Additionally, for higher frequencies, the gain is much lower and hence measuring the input signal at the output of U3 would give an inaccurate measurement for the gain.

8.19

The gain of an inverting amplifier can be computed by :

$$G = \left| \frac{V_{out}}{V_+ - V_-} \right| = \left| \frac{V_{out}}{V_-} \right| \quad (4)$$

We consider the behavior of the circuit in question 8.12, and compute the gain and averaged the value over the frequency range 10^2 to 10^7 Hz and obtain a gain of around 5149. Our result don't quite correspond to the gain computed in 8.17, which had smaller (≈ 1000) gain values.

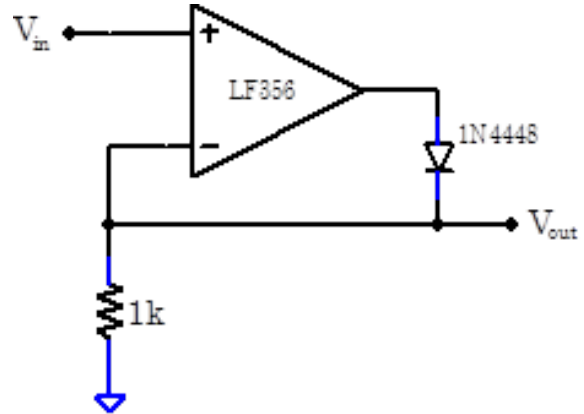


Figure 28: Circuit Schematic for the active rectifier.

8.20

We build the active rectifier circuit as shown in Fig.28. The circuit rectifies well at low frequencies. Fig.29 depicts the distortion on the output signal we saw when we fed in a 50kHz triangular wave.

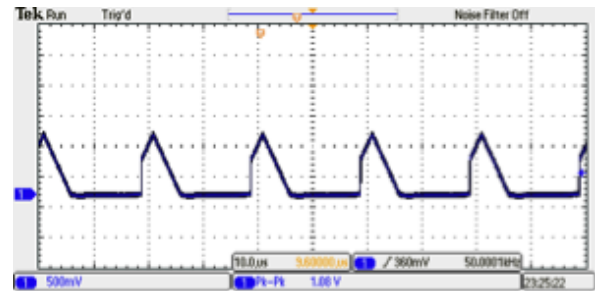


Figure 29: Triangular wave distortion at high frequencies.

When we reconnected the scope to measure the output of the op amp, we found that the scope trace looks as depicted in Fig.30. For negative portions of the signal the op-amp immediately switches and rails because there is no feedback present for the negative part of signal due to the diode only being forward conducting.

We improve the rectifying circuit by adding an additional diode as shown in Fig.31. We found that the output did not rail for the pos-

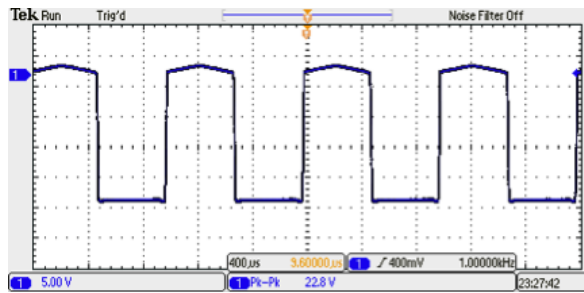


Figure 30: Output of the op amp. The op-amp rails for the negative portion of the input.

itive portions of the signal, as shown in Fig.32.

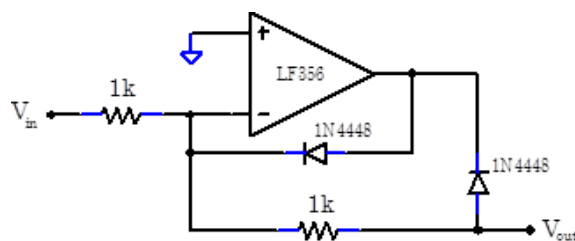


Figure 31: Improved rectifying circuit.

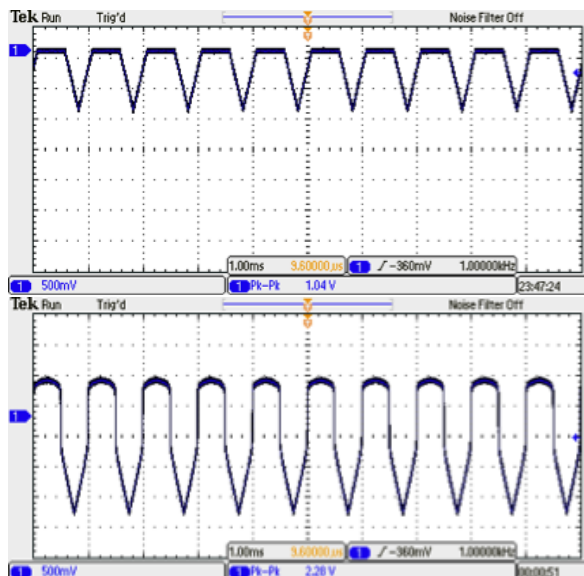


Figure 32: Scope trace from improved circuits. Bottom: The trace taken at output of op-amp. The op-amp doesn't rail for positive part of signal because there are now 2 diodes in the feedback loop to account for signals that are both positive and negative.

Conclusion

In this lab, we examine situations where the function of op-amps is limited and scenarios where the op-amp golden rules are violated. We investigate possible sources of errors such as Johnson noise and input bias currents. In addition, we continue to explore applications of op-amps by building advanced circuits such as the bipolar follower and the push-pull circuit.

Acknowledgments

The author would like to acknowledge support from the GSI in this lab in addressing our questions about the lab and with the handling of liquid nitrogen. I would also like to thank my partner, Leah Tom, for helpful discussion and collaboration that helped this work. We also appreciate Alan Luu for providing us with guidance on question 8.18.

References

- Horowitz, Paul, and Winfield Hill. *The Art of Electronics*. Cambridge: Cambridge UP, 1989. Print.
- "Crossover Distortion." *Wikipedia*. Wikimedia Foundation, n.d. Web. 02 Apr. 2015.
- "Lab 8 - Op Amps III." *Donald A. Glaser Advanced Lab*. Regents of the University of California, n.d. Web. 29 Mar. 2015.

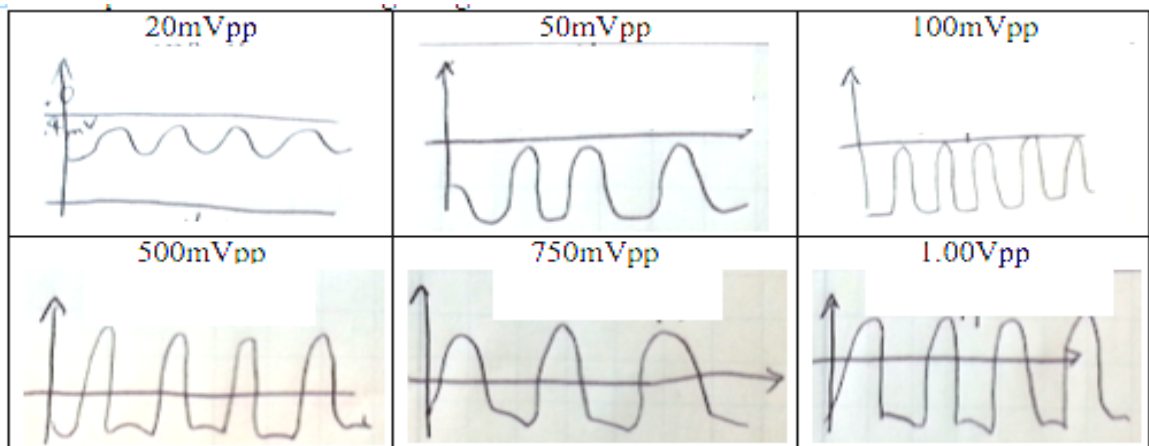


Figure 6: Sketches of output waveforms with corresponding input amplitudes.

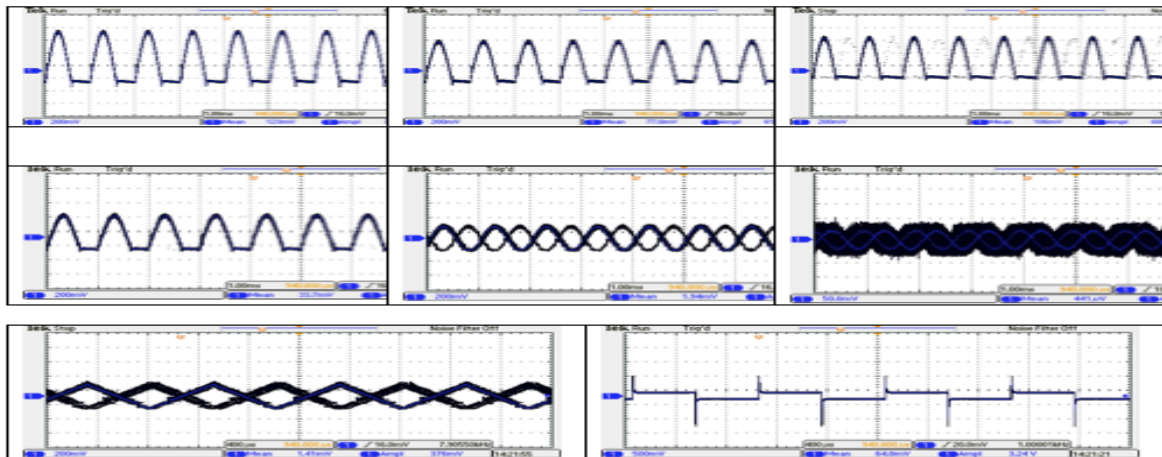


Figure 7: Sketches of output wave forms arranged with increasing input amplitudes towards the right. Top row features the triangular wave which is rectified but not distorted. Middle row shows the increasing distortion as amplitude is increased for the sinusoidal waveform. Likewise, the bottom row shows distortion for the square waveform.

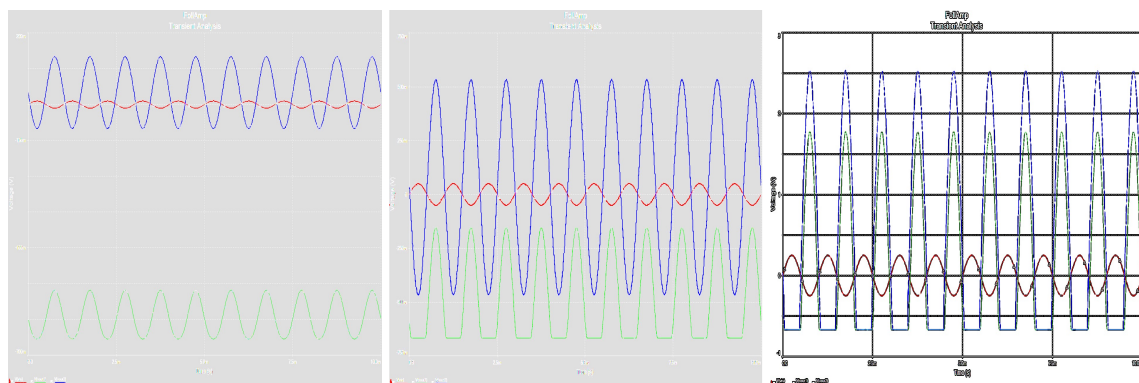


Figure 8: Multisim simulation result for V_{in} of 0.01 (Left), 0.05 (Middle) and , 0.25V (Right). Red: Input waveform. Green: Output waveform for the 8.6 circuit. Blue: Output waveform for the 8.7 circuit.

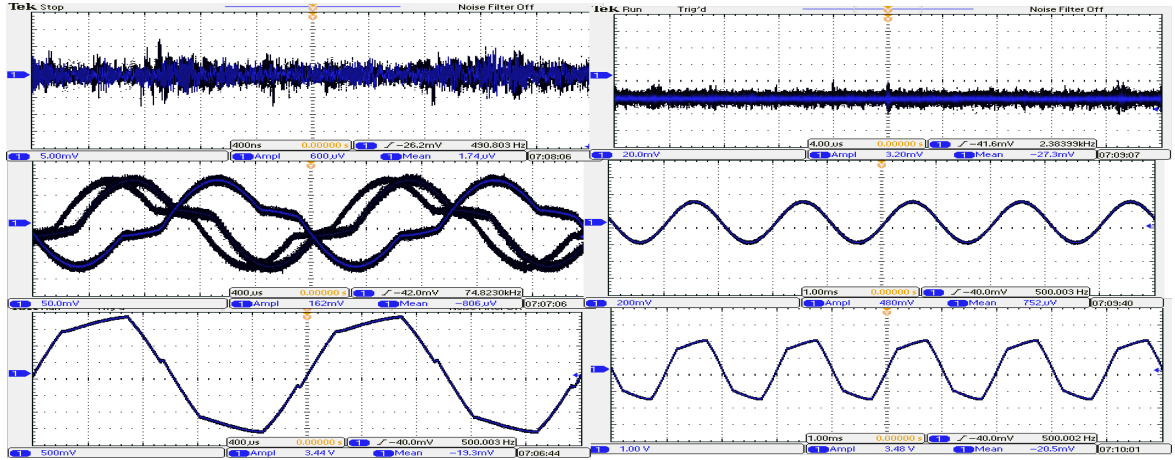


Figure 10: Crossover distortion in for an input wave amplitude of 0.015 (Top) ,0.15 (Middle) and 1.5 V_{pp}(Bottom). The left panels show the signal behaviour for the Fig.9 circuit, right panels for the second circuit in Fig. 11.

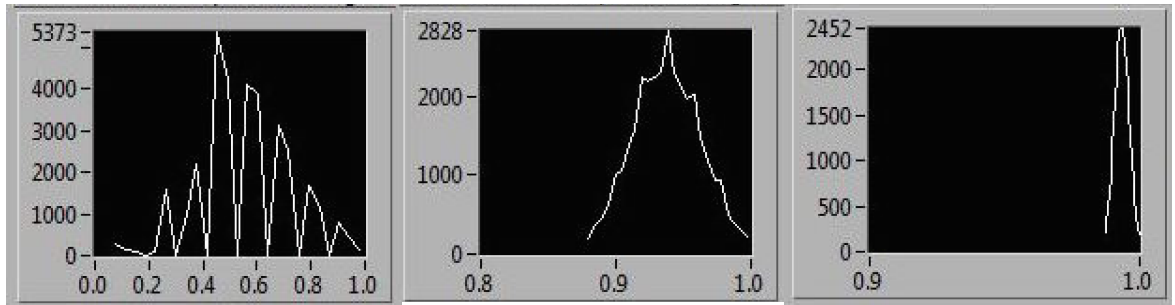


Figure 16: Left: N = 10; Middle: N=1000 ; Right N=10000. [Real-time data amplitude histogram; x: amplitudes ; y: counts] When we set the average number of shots per sample to larger numbers the spectrum looks more Gaussian and shifts towards the 1.0.

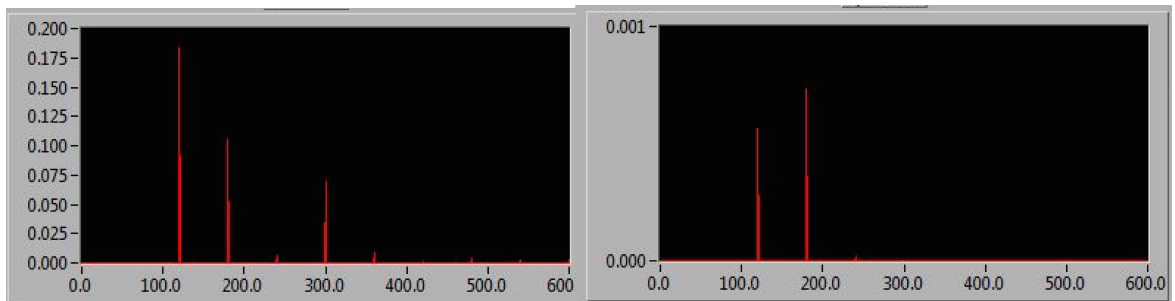


Figure 17: Decomposed spectrum for the noise signal. Left: Harmonic content 0.2; Right: Harmonic Content: 0.8 . [x: frequency ; y: number of shots]