

$$V = I R_{eq} = I (R_1 + R_2)$$

$$I = \frac{V}{R_1 + R_2}$$

$$V_A = \frac{V R_2}{R_1 + R_2}$$



We build a voltage divider s.t. $R_1 = 470 \text{ k}\Omega$
 $R_2 = 10 \text{ k}\Omega$; $V = 24 \text{ V}$

1.5)

$$I = \frac{V}{R_1 + R_2} = \frac{24 \text{ V}}{(470 \times 10^3) \Omega} = 5.0 \times 10^{-5} \text{ A}$$

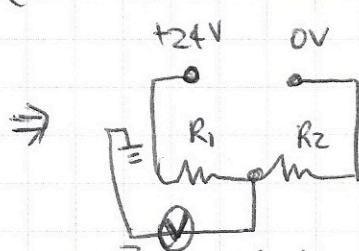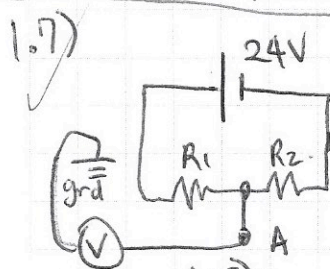1.6)

$$V_A = \frac{(24 \text{ V})(10 \times 10^3)}{(470 \times 10^3 + 10 \times 10^3)} = 0.5 \text{ V}$$



1.8) Actual resistance $R_1 = 465.6 \text{ k}\Omega$
 $R_2 = 9.89 \text{ k}\Omega$
 Actual voltage $V = 24.589 \text{ V}$

within the 5% tolerance (specified by the gold band)

$$\delta R_1 = 4.4 \text{ k}\Omega \rightarrow 0.94\%$$

$$\delta R_2 = 0.11 \text{ k}\Omega \rightarrow 1.1\%$$

tolerance $\sim 2.45\%$ (within tolerance level)

we correct the DMM to ground on one terminal and A at the other the mistake that we made was that we fed the +24V to R_2 and 0V terminal to R_1 . This caused us to get $\sim 24 \text{ V}$, because $24 - 0.5$ is $\sim 23.5 \text{ V}$

1.7a) to measure current thru the $10 \text{ k}\Omega$ resistor connect in parallel and measure the V across the resistor. Using the nominal value we find that

b)

$$I = \frac{V}{R} = \frac{0.510 \text{ V}}{10 \text{ k}\Omega} = 0.000051 \text{ A}$$

\approx Same as predicted in 1.5)

1.9)

$$I = \frac{24.589 \text{ V}}{(465.6 + 9.89) \text{ k}\Omega} = 0.0000517 \text{ A} = 0.0517 \text{ mA}$$

$V_A = \frac{(24.589 \text{ V})(9.89 \text{ k}\Omega)}{(465.6 + 9.89) \text{ k}\Omega} = 0.5114 \text{ V}$

1.10)

$$V_A = 0.51086 \text{ V}$$

accuracy = $0.012\% (0.51086 \text{ V}) + 0.004\% \cdot 1 \text{ V}$
 $= 1.013068 \times 10^{-4} \text{ V}$

So the $0.51086 \text{ V} \pm 0.13068 \text{ mV}$

Our measurement is not within the range but if we round to 2 significant figures then it will fall within the range.

1.12) a)

$$P_1 = I V = \frac{V^2}{R_1} = \frac{(24 \text{ V})^2}{470 \text{ k}\Omega} = 1.226 \times 10^{-3} \text{ W}$$

power dissipated from R_1

$P_2 = \frac{(24 \text{ V})^2}{10 \text{ k}\Omega} = 5.76 \times 10^{-2} \text{ W}$

this makes sense \because it should be less than quarter watt.

b) decrease R value so that more current pass thru ($\because P = I^2 R$)

c) The $10 \text{ k}\Omega$ resistor would reach the max power rating first

1.11) Current through $R_1 = \frac{24.072 \text{ V}}{470 \text{ k}\Omega}$
 Current through $R_2 = \frac{0.51079 \text{ V}}{9.89 \text{ k}\Omega}$

$I_1 = 5.1217 \times 10^{-5} \text{ A}$
 $I_2 = 5.1671 \times 10^{-5} \text{ A}$

Note: ammeter must be connected in series & prong need to be on the bottom two

1.11) Current Directly measured by DMM

$$I_A = 0.0030 \text{ mA}$$

d)

$$P = \frac{V^2}{R} = 0.25 \text{ W} = \frac{(24 \text{ V})^2}{R}$$

$R = 2.304 \text{ k}\Omega$
 make it approximately 200 times smaller

e) we can arrange several resistors in parallel to decrease its effective resistance but in practice we would require a lot of parallel resistor so will be hard to build.

SIGNATURE

DATE

WITNESS/TA

1.20)

Oscilloscope: V_{rms}	Frequency (Hz)	10	31.6	100	316	1000	3160	10000	31600	100000	200000
		480×10^{-3}	480×10^{-3}	480×10^{-3}	480×10^{-3}	480×10^{-3}	480×10^{-3}	480×10^{-3}	485×10^{-3}	485×10^{-3}	485×10^{-3}

b/w 39 & 40 Hz


freq (Hz)	316000	300,000	1 MHz	3 MHz	5 MHz	6 MHz	7 MHz	5.5 MHz
	485×10^{-3}	490×10^{-3}	490×10^{-3}	490×10^{-3}	495×10^{-3}	1.02	1.03	1.015

freq (Hz)	7.5 MHz	8.0 MHz	8.5 MHz	9.0 MHz	9.5 MHz	10 MHz
$V_o (V)$	1.04	1.06	1.06	1.08	1.09	1.10

DMM:

freq (Hz)	10	31.6	100	316	1000	3160	10000	31600	100000	316000	1 MHz	2 MHz
$V_o (V)$	0.35388	0.35382	0.35377	0.35356	0.35329	0.35319	0.35331	0.35342	0.35360	0.36220	0.51622	0.56538

freq	2.25 MHz	2.5 MHz	3 MHz	3.1 MHz
$V_o (V)$	32.921 mV	18.133 mV	3.925 mV	1.634 mV

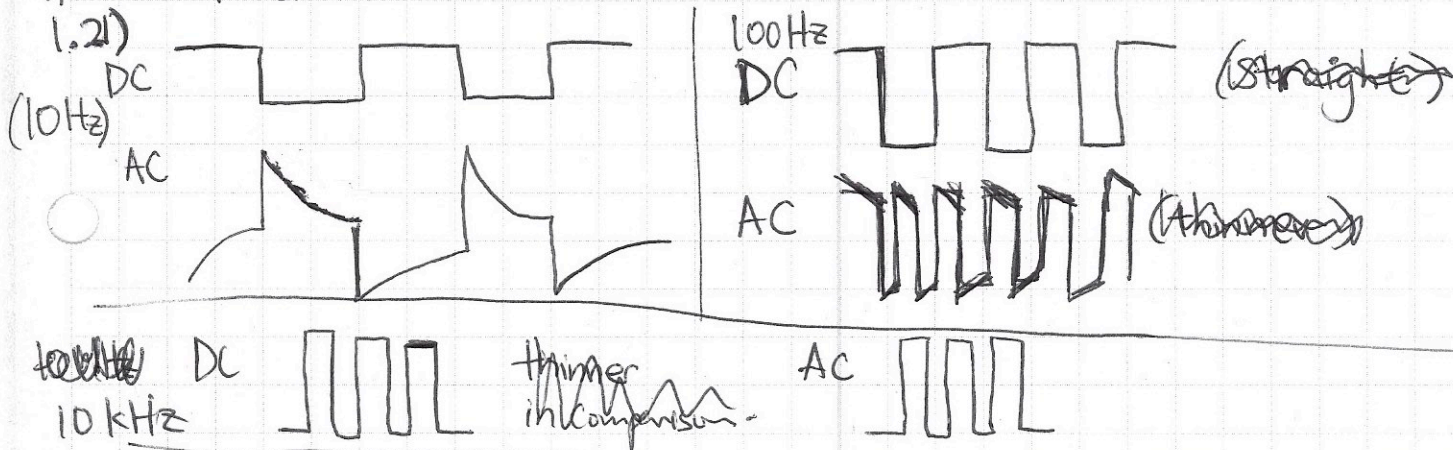

The reason why the AC signal looks weird in the lower frequencies is that since there are fewer cycles in the same amount of sampling time the average is less accurate. What the AC does is that it subtracts off the average value from the DC signal. So if the average value is not the actual mean then subtracting this off will result in the weird waveform as seen in the 10 Hz & 100 Hz AC signals.

Note: the 50 Ω terminator introduces noise to the scope reading. So we didn't use it in our measurement. Instead we set Output Menu \rightarrow Impedance \rightarrow High Z for the terminator effect instead.

EXP. NUMBER	EXPERIMENT/SUBJECT Signature Page	DATE	
NAME Jung Lin Lee (Doris)	LAB PARTNER Leah Tom	LOCKER/DESK NO.	COURSE & SECTION NO. 63

Prelab Part I

[Signature]

Problem 1.1.13

Xiaofei Zhou

1.15

[Signature]

1.18

[Signature]

1.21

[Signature]

[Signature]

Prelab Part II

[Signature]

1.2.2

[Signature]

1.2.7

1.2.8

[Signature]

COPY

SIGNATURE	DATE	WITNESS/TA	DATE
-----------	------	------------	------

EXP. NUMBER	EXPERIMENT/SUBJECT	DATE	
NAME	LAB PARTNER	LOCKER/DESK NO.	COURSE & SECTION NO.

60

1.20)

oscilloscope: V_{out}

frequency (Hz)	10	31.6	100	316	1000	3160	10000	31600	100000	200000
	480×10^3	480×10^3	480×10^3	480×10^3	480×10^3	480×10^3	480×10^3	485×10^3	485×10^3	485×10^3

b/w 39 & 40 Hz


freq (Hz)	316000	300,000	1 MHz	3 MHz	5 MHz	6 MHz	7 MHz	5.5 MHz
V	485×10^{-3}	490×10^{-3}	490×10^{-3}	490×10^{-3}	495×10^{-3}	1.02	1.03	1.015

freq (Hz)	7.5 MHz	8.0 MHz	8.5 MHz	9.0 MHz	9.5 MHz	10 MHz
V_o (V)	1.04	1.06	1.06	1.08	1.09	1.10

DMM:

freq (Hz)	10	31.6	100	316	1000	3160	10000	31600	100000	316000	1 MHz	2 MHz
V_o (V)	0.35388	0.35382	0.35377	0.35356	0.35329	0.35319	0.35331	0.35342	0.35360	0.36220	0.51622	0.56538

freq (Hz)	2.25 MHz	2.5 MHz	3 MHz	3.1 MHz
V_o (V)	32.92 mV	18.133 mV	3.925 mV	1.634 mV

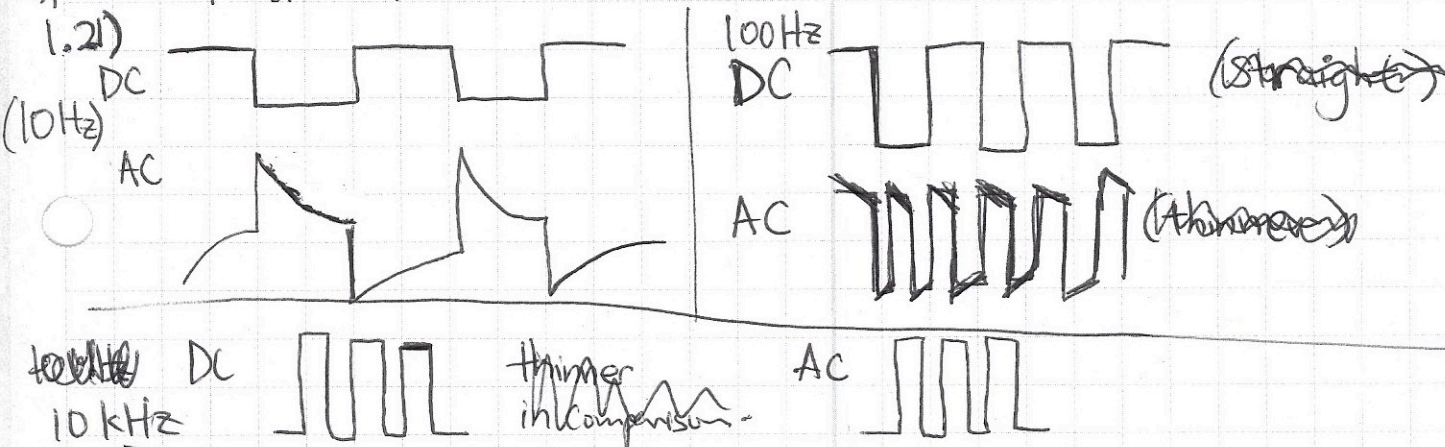

The reason why the AC signal looks weird in the lower frequencies is that since there are fewer cycles in the same amount of sampling time the average is less accurate. What the AC does is that it subtracts off the average value from the DC signal. So if the average value is not the actual mean then subtracting this off will result in the weird waveform as seen in the 10 Hz & 100 Hz AC signals.

Note: the 50 Ω terminator introduces noise to the scope reading. So we didn't use it in our measurement. Instead we set Output Menu \rightarrow Impedance \rightarrow High Z for the terminator effect instead.

SIGNATURE	DATE	WITNESS/TA	DATE
-----------	------	------------	------

EXP. NUMBER	EXPERIMENT/SUBJECT	DATE	65
NAME	LAB PARTNER	LOCKER/DESK NO.	COURSE & SECTION NO.

for $10k\Omega$:

$$R = \frac{1}{\frac{1}{3.1367} + \frac{1}{10}} = 2.387k\Omega$$

$$I = \frac{V}{R} = \frac{9V}{2.387k\Omega} = 3.77mA$$

for 100Ω :



$$R = \frac{1}{\frac{1}{100} + \frac{1}{3136.7}} = 96.91\Omega$$

$$I = \frac{9V}{96.91\Omega} = 92.87mA$$

$$R = 0.0067M\Omega$$

after shorted across the 2 terminal
across any terminal need to $\div 2$
Ignoring the voltage sources


$$\Rightarrow R = 0.00335M\Omega$$

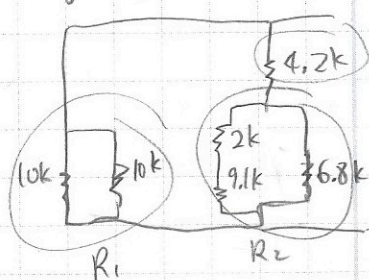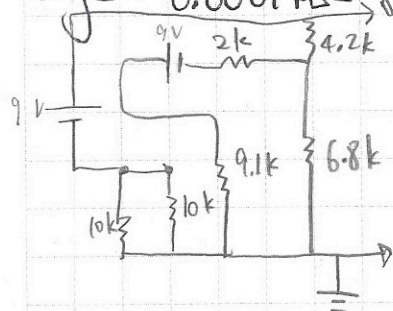

$$R_1 = \frac{1}{\frac{1}{10} + \frac{1}{10}} = \frac{1}{\frac{2}{10}} = 5k\Omega \approx 0.0034M\Omega$$

$$\Rightarrow R_2 = \frac{1}{\frac{1}{2+9.1} + \frac{1}{6.8}} = 4.2167k\Omega$$

$$R_3 = 4.2k\Omega$$

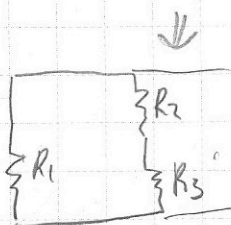

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2+R_3}} = \frac{1}{\frac{1}{5} + \frac{1}{8.4167}} = 3.1367k\Omega$$

Ignoring all the resistors \Rightarrow in parallel $V_{eq} \approx 9V$

for the $1k\Omega$

Before the measurements

$$R = \frac{1}{\frac{1}{3.1367k} + \frac{1}{1k}} = 957\Omega$$

$$I = \frac{V}{R} = \frac{9V}{957\Omega} = 0.01187A$$

	100Ω	$1k\Omega$	$10k\Omega$
V_{th}	0.1440V	1.131V	3.585V
I_{th}	1.448mA	1.138mA	0.3625mA

SIGNATURE	DATE	WITNESS/TA	DATE
-----------	------	------------	------